

# **CPE166 Advanced Logic Design**

## **Lab 2 Report**

**Student Name: Andy Cha**

**Date: 3-06-2020**

**California State University, Sacramento**

## TABLE OF CONTENTS

Section	Page
Title Page .....	1
Table Of Contents .....	2
1. Introduction .....	3
2. Part 1: 8-bit Carry Select Adder Design .....	4
Part 1.1: 1 Half Adder Source Code, Testbench & Simulation Waveform.....	4
Part 1.2: Full Adder Source Code, Testbench & Simulation Waveform.....	5
Part 1.3: 8-Bit Carry Select Adder Code, Testbench & Simulation Waveform.....	6
Part 1.4: Multiplexer(MUX) Code, Testbench & Simulation Waveform.....	7
Part 1.5: Multiplexer(MUXB) Code, Testbench & Simulation Waveform.....	8
Part 1.6: 8-bit Carry Select Adder Code, Testbench & Simulation waveform.....	9
Part 1: 8-bit Carry Select Adder Result Discussion.....	11
3. Part 2: 4 By 4 Binary Sequential Multiplier Design.....	12
Part 2.1: Design Purpose.....	12
Part 2.2: Design Code.....	13-17
Part 2.2: Design Code & Result Discussion.....	17
4. Part 3: Character Displays on 8-Digit Multiplexed Seven Segment Displays.....	18
Part 3.1: Design Purpose.....	19
Part 3.2: Design Code.....	20
Part 3.2: Design Code & Result Discussion.....	20
5. Conclusion.....	21

## **Introduction**

In this lab we will work with Carry select adder, sequential multiplier, and multiplexed seven segment displays. The purpose of this lab is to give us practice in hierarchical design and design strategy using Verilog. We must be familiar with how carry select adder works, sequential shift/add multiplication algorithm and multiplexed seven segment display. Once we understand how those 3 work, we can simulate the design with waveforms and determine if it is working. Then we will apply our Verilog code into the FPGA setting up the pins allocated to each input and output.

## Part 1: 8-bit Carry Select Adder Design


### Part 1.1

The first part of this lab we will need to create a half adder first. The truth table is given to us along with the design. From this we can create our Verilog code along with the testbench.

Truth Table

Inputs		Outputs	
A	B	C <sub>out</sub>	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

 Logic Equations:  
 $C_{out} = A \& B$   
 $Sum = A \oplus B$



Source Code:

half\_adder - Notepad

File Edit Format View Help

```
module half_adder(a, b, cout, sum);
input a, b;
output cout,sum;
assign cout = a & b;
assign sum = a ^ b;
endmodule
```

half\_adder\_tb - Notepad

File Edit Format View Help


```
module half_adder_tb;
reg a, b;
wire cout, sum;

half_adder u1(.a(a), .b(b), .cout(cout), .sum(sum));

initial
begin


a=0; b=0;
#10
a=0; b=1;
#10
a=1; b=0;
#10
a=1; b=1;
#20 $stop;
end

endmodule
```

 
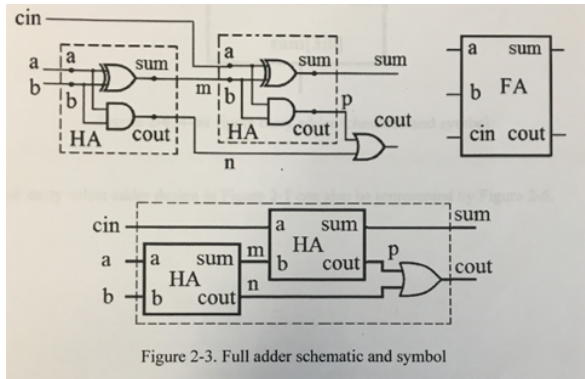
## Part 1.2

Once we have created the half adder we can use it to create a full adder. A full adder consists of 2 half adders and one OR gate.



Truth Table

Inputs			Outputs	
A	B	C <sub>in</sub>	C <sub>out</sub>	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Logic Equations:  
 $Sum = A \oplus B \oplus C_{in}$   
 $C_{out} = (A \oplus B) C_{in} + A \& B$

Source Code:

full\_adder - Notepad

```
File Edit Format View Help
module full_adder(a, b, cin, cout, sum);
input a, b, cin;
output cout, sum;
wire m, n, p;


half_adder g1(.cout(n), .sum(m), .a(a), .b(b));
half_adder g2(.cout(p), .sum(sum), .a(cin), .b(m));
or g3(cout, p, n);

endmodule
```

full\_adder\_tb - Notepad


```
File Edit Format View Help
module full_adder_tb;
reg a, b, cin;
wire cout, sum;
full_adder u1(.a(a), .b(b), .cin(cin), .cout(cout), .sum(sum) );

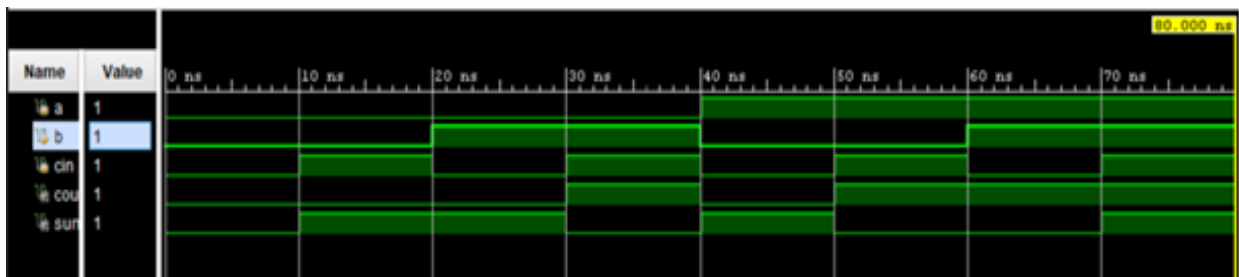initial
begin
{a, b, cin} = 3'b000;
#10 {a, b, cin} = 3'b001;
#10 {a, b, cin} = 3'b010;
#10 {a, b, cin} = 3'b011;
#10 {a, b, cin} = 4;
#10 {a, b, cin} = 5;
#10 {a, b, cin} = 6;
#10 {a, b, cin} = 7;
#10 $stop;
end
```


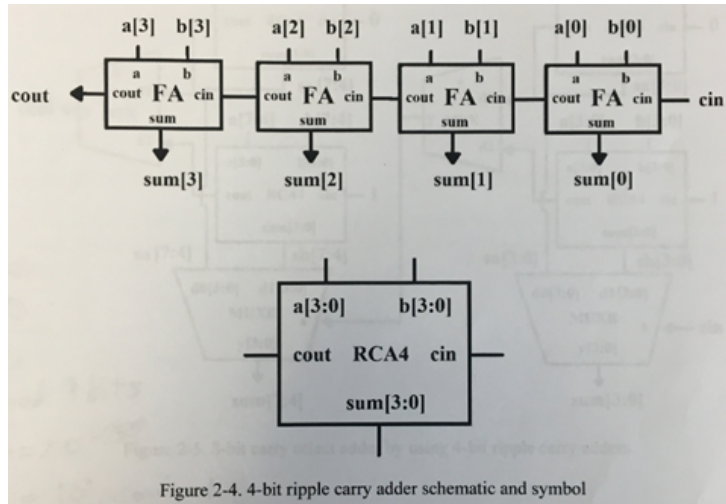
## Part 1.3

Once we have the full adders completed we have to create a 4-bit ripple carry adder(RCA4). We connect 4 full adders together and move the cout to the next full adder's cin. We also have to change inputs to [3:0] a, b and create a name for the wires in the middle which will be [3:0] m.



Source Code:

fa\_ripplecarry - Notepad

File Edit Format View Help

```
module fa_ripplecarry(a, b, cin, cout, sum);
input [3:0] a, b;
input cin;
output [3:0] sum;
output cout;

wire [3:0] m;

full_adder g1(.cout(m[0]), .sum(sum[0]), .cin(cin), .a(a[0]), .b(b[0]) );
full_adder g2(.cout(m[1]), .sum(sum[1]), .cin(m[0]), .a(a[1]), .b(b[1]) );
full_adder g3(.cout(m[2]), .sum(sum[2]), .cin(m[1]), .a(a[2]), .b(b[2]) );
full_adder g4(.cout(cout), .sum(sum[3]), .cin(m[2]), .a(a[3]), .b(b[3]) );

endmodule
```

fa\_ripplecarry\_tb - Notepad


File Edit Format View Help

```
module fa_ripplecarry_tb;
reg[3:0] a, b;
reg cin;
wire [3:0] sum;
wire cout;
wire [3:0] res;

assign res = { cout, sum };

fa_ripplecarry u1( a, b, cin, cout, sum );
initial
begin
a = 2; b = 4; cin = 0;
#10 a = 3; b = 3; cin = 1;
#10 a = 5; b = 6; cin = 1;
#10 a = 7; b = 7; cin = 1;
#10 $stop;
end

endmodule
```

 

## Part 1.4

Here we will use the multiplexer that was created in Lab 1.

 


Table 2-3. MUX truth table

Input	Output
s	y
0	d0
1	d1

Source Code:

mux - Notepad

```
File Edit Format View Help
module mux(d0, d1, s, y);
input d0, d1;
input s;
output y;
wire m,n;

assign m = (~s)&d0;
assign n = s & d1;
assign y = m | n;

endmodule
```

mux\_tb - Notepad

```
File Edit Format View Help
module mux_tb;
reg[1:0]d;
reg s;
wire y;
mux2to1 u1(.d(d), .s(s), .y(y));
initial
begin

    d=2'b10; s=0;
    #10;
    d=2'b01; s=0;
    #10;
    d=2'b10; s=1;
    #10;
    d=2'b01; s=1;
    #20 $stop;

end
endmodule
```




## Part 1.5

Here We will use the multiplexer that was created from Lab 1. We have to modify it to take 4 bits instead of one bit. We can use the same Testbench as the mux but we need to change the instance name to "muxb" and change the inputs to 4 bits. Then we also need to include a cin.

Table 2-4. MUXB truth table

Input	Output
s	y[3:0]
0	d0[3:0]
1	d1[3:0]

 


Source Code:

muxb - Notepad

File Edit Format View Help
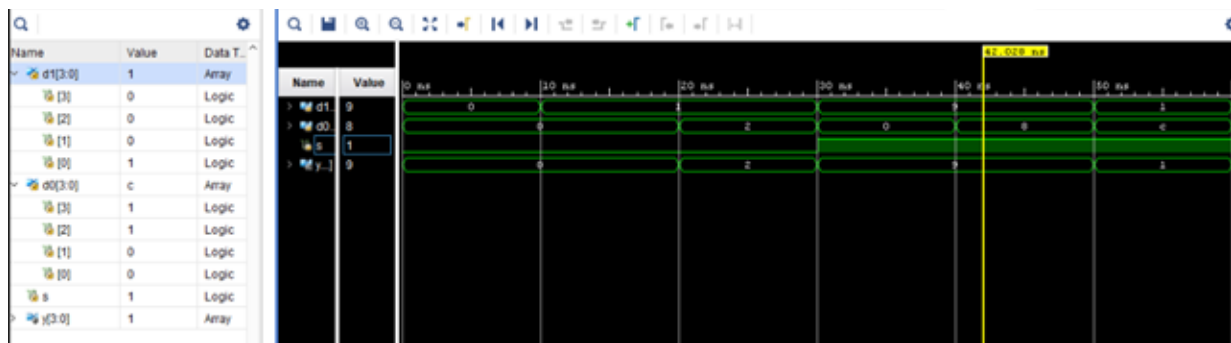
```
module muxb(d0, d1, s, y);
input [3:0] d0;
input [3:0] d1;
input s;
output [3:0] y;
reg [3:0] y;
always@(s)
begin
if(s > 0)
y <= d1;
else
y <= d0;
end
endmodule
```





## Part 1.6

Now we have all the components we need, we can design the carry select adder(CSA8) by connecting 4 RCA4, 2 MUXB, and 2 MUX. In Verilog we can make 8 instances and connect each one with the correct wires.

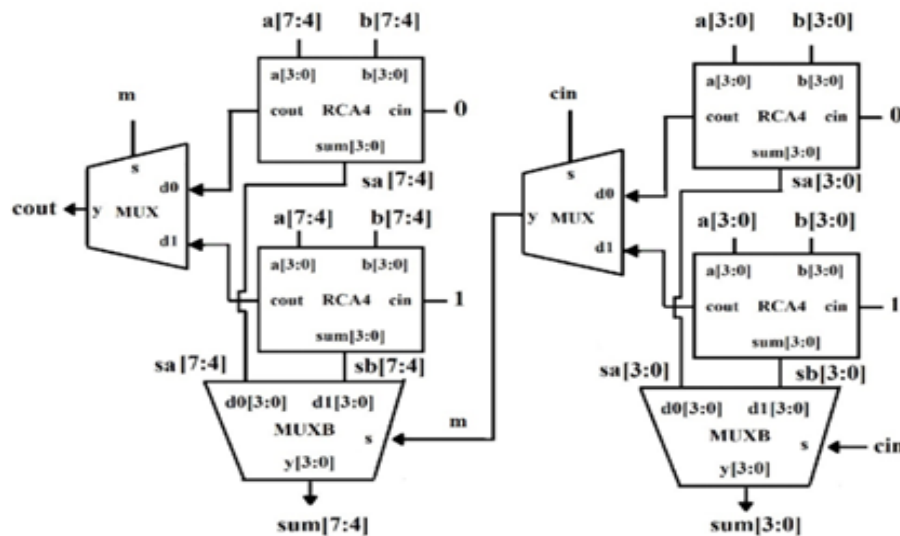


Figure 2-5. 8-bit carry select adder by using 4-bit ripple carry adders

## Source Code:

cs8.demo - Notepad

```
File Edit Format View Help
module csa8(a, b, cin, cout, sum);
input [7:0] a, b;
input cin;
output [7:0] sum;
output cout;
wire [3:0] z;
wire m;
wire [7:0] sa;
wire [7:0] sb;

fa_ripplecarry g1(.cout(z[0]), .sum(sa[3:0]), .cin(0), .a(a[3:0]), .b(b[3:0]) );
fa_ripplecarry g2(.cout(z[1]), .sum(sb[3:0]), .cin(1), .a(a[3:0]), .b(b[3:0]) );
muxb g3(.d0(sa[3:0]), .d1(sb[3:0]), .s(cin), .y(sum[3:0]) );

mux g4(.d1(z[1]), .d0(z[0]), .s(cin), .y(m) );

muxb g5(.d0(sa[7:4]), .d1(sb[7:4]), .s(m), .y(sum[7:4]) );
fa_ripplecarry g6(.cout(z[2]), .sum(sa[7:4]), .cin(0), .a(a[7:4]), .b(b[7:4]) );
fa_ripplecarry g7(.cout(z[3]), .sum(sb[7:4]), .cin(1), .a(a[7:4]), .b(b[7:4]) );
mux g8(.d1(z[3]), .d0(z[2]), .s(m), .y(cout) );

endmodule
```

csa8\_tb - Notepad


```
File Edit Format View Help
module csa8_tb;
reg[7:0] a, b;
reg cin;
wire [7:0] sum;
wire cout;

csa8 u1( a, b, cin, cout, sum);

initial
begin
a = 8'b0000_0001; b = 8'b1000_0011; cin = 1'b0;
#10
a = 8'b0100_0101; b = 8'b1100_0001; cin = 1'b1;
#10
a = 8'b1010_1010; b = 8'b0101_0101; cin = 1'b0;
#10
a = 8'b0000_1111; b = 8'b1111_0000; cin = 1'b1;
#10 $stop;

end

endmodule
```

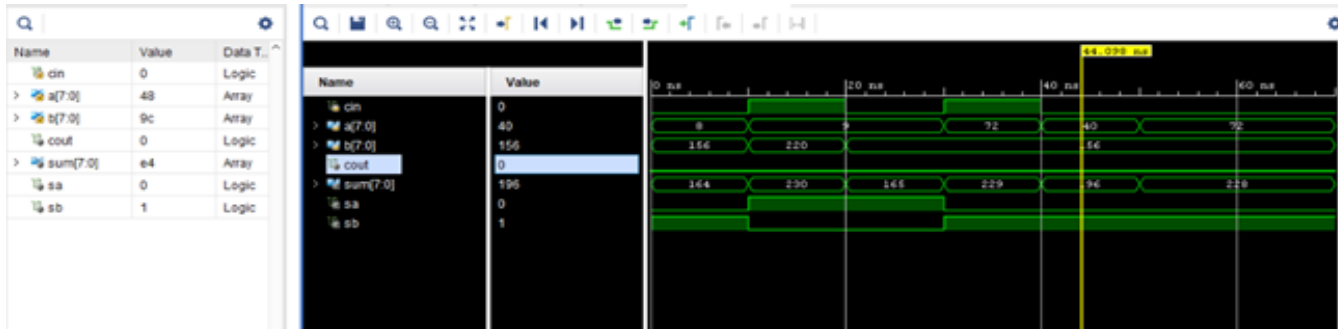

### Result Discussion:

The result of this part was that the CSA8 adds two 8-bit numbers properly. It took a lot of time designing all the Verilog files and creating testbenches for each one to determine that there were no issues with it. It was better to check each piece to see if it was right than to test the final product and guess where the error was out of all the files. Some issues I came across were creating the CSA8. Putting all the files together took some time and had to overlook the diagram over and over. The goal of this part was how to use combinational logic and putting it together to create an 8 bit carry adder.



## Part 2.2:

### Source Code:

```

module adder (a, b, cout, sum,);
input  [3:0] a, b;
output [3:0] sum;
output cout;

assign {cout,sum} = a + b;
endmodule

module adder_tb;
reg  [3:0] a;
reg  [3:0] b;
reg  clk;
reg  add;
wire  cout;
wire  [3:0]sum;
adder u1(.a(a), .b(b), .cout(cout), .sum(sum), .clk(clk), .add(add));

initial clk = 1;
always #10 clk = ~clk;
initial
begin
add = 0;
a = 4'b0000; b = 4'b0000;
#15;
add=1; a = 4'b1101; b = 4'b1110;
#20;
add=0; a = 4'b0001; b = 4'b0000;
#20;
add = 1;
#20;
add = 0; a = 4'b1000; b = 4'b1011;
#20;
add=1;
#20 $stop;
end

endmodule

```

dffa - Notepad
File Edit Format View Help

```

module dffa (clr, clk, ld, da, qa);
input clr, clk, ld;
input [3:0] da;
output [3:0] qa;

reg [3:0] qa;

always@(posedge clk or posedge clr)
begin
if(clr)
    qa <= 4'b0000;
else if(ld)
    qa <= da;
end
endmodule

```

dffa\_tb - Notepad
File Edit Format View Help

```

module dffa_tb;
reg clr, clk, load;
reg [3:0] da;
wire [3:0] qa;

dffa u1(.clr(clr), .clk(clk), .load(load), .da(da), .qa(qa));

initial clk = 0;
always #10 clk = ~clk;

initial
begin
clr = 1; load = 0; da = 4'b1010;
#10 clr = 0;
load = 1;
#10;
load = 0;
#10;
clr = 1;
#10;
$stop;

end

endmodule

```

```

module dffb (clr, clk, ld, shb, db, qb)
input clr, clk, ld, shb;
input [3:0] db;
output [3:0] qb;

reg [3:0] qb;

always@(posedge clk or posedge clr)
begin
if(clr)
qb <= 4'b0000;
else if(ld)
qb <= db;
else if (shb)
qb <= { 1'b0, qb[3:1] };
end
endmodule

module dffb_tb;
reg clk, clr, load, shift;
reg [3:0] db;
wire [3:0] qb;

dffb u1(.clr(clr), .clk(clk), .load(load), .shift(shift), .db(db), .qb(qb));

initial clk = 0;
always #10 clk = ~clk;

initial
begin
clr = 1; load = 0; shift = 0; db = 4'b1010;
#10 clr = 0;
load = 1;
#10;
load = 0; shift = 1;
#50;
clr = 1;
#10;
$stop;
end
endmodule

```

```

module fsm(reset, clk, clr, shb, ld, ldp, shp);
input reset, clk;
output clr, shb, ld, ldp, shp;

reg clr, shb, ld, ldp, shp;
reg[3:0] cs, ns;

parameter s0 = 4'b0000, s1 = 4'b0001, s2 = 4'b0010, s3 = 4'b0011, s4 = 4'b0100,
s5 = 4'b0101, s6 = 4'b0110, s7 = 4'b0111, s8 = 4'b1000,
s9 = 4'b1001, s10 = 4'b1010, s11 = 4'b1011, s12 = 4'b1100;

always @ (posedge clk or posedge reset)
begin
if(reset)
cs <= s0;
else
cs <= ns;
end

always @ (cs)
begin
case(cs)
s0: ns = s1;
s1: ns = s2;
s2: ns = s3;
s3: ns = s4;
s4: ns = s5;
s5: ns = s6;
s6: ns = s7;
s7: ns = s8;
s8: ns = s9;
s9: ns = s10;
s10: ns = s11;
s11: ns = s12;
s12: ns = s12;
default: ns = s0;
endcase
end

```

```

always @ (cs)
begin
    case(cs)
        s0: begin
            clr = 1; ld = 0; shp = 0; shb = 0; ldp = 0;
        end
        s1: begin
            clr = 0; ld = 1; shp = 0; shb = 0; ldp = 0;
        end
        s2: begin
            clr = 0; ld = 0; shp = 0; shb = 0; ldp = 1;
        end
        s3: begin
            clr = 0; ld = 0; shp = 1; shb = 0; ldp = 0;
        end
        s4: begin
            clr = 0; ld = 0; shp = 0; shb = 1; ldp = 0;
        end
        s5: begin
            clr = 0; ld = 0; shp = 0; shb = 0; ldp = 1;
        end
        s6: begin
            clr = 0; ld = 0; shp = 1; shb = 0; ldp = 0;
        end
        s7: begin
            clr = 0; ld = 0; shp = 0; shb = 1; ldp = 0;
        end
        s8: begin
            clr = 0; ld = 0; shp = 0; shb = 0; ldp = 1;
        end
        s9: begin
            clr = 0; ld = 0; shp = 1; shb = 0; ldp = 0;
        end
        s10: begin
            clr = 0; ld = 0; shp = 0; shb = 1; ldp = 0;
        end
        s11: begin
            clr = 0; ld = 0; shp = 0; shb = 0; ldp = 1;
        end
        s12: begin
            clr = 0; ld = 0; shp = 0; shb = 0; ldp = 0;
        end

        default: begin
            clr = 0; ld = 0; shp = 0; shb = 0; ldp = 0;
        end
    endcase
end
endmodule

```

mux - Notepad

File Edit Format View Help

module mux(s, a, b, y);

input [3:0] a, b;

input s;

output [3:0] y;

assign y = s? b : a;

endmodule

mux\_tb - Notepad

File Edit Format View Help

module mux\_tb;

reg[3:0] a, b;

reg s;

wire [3:0] y;

mux u1(.s(s), .a(a), .b(b), .y(y));

initial

begin

a = 4'b1100; b = 4'b0011; s = 0;

#10;

a = 4'b1100; b = 4'b0011; s = 1;

#20;

\$stop;

end

endmodule

preg - Notepad

File Edit Format View Help

module preg(sum, shp, ldp, clr, p, clk, cout);

input clk, clr, ldp, shp, cout;

input [3:0] sum;

output [7:0] p;

reg [7:0] p;

always @ (posedge clk or posedge clr)

begin

if (clr)

p &lt;= 8'b0000;

else if (ldp)

p[7:3] &lt;= {cout, sum};

else if (shp)

begin

p[7:3] &lt;= {1'b0, p[7:4]};

p[2:0] &lt;= {p[3], p[2:1]};

end

end

endmodule

```

module mult(db,da,p,clk,ld,shb,clr,shp,ldp);
input clk, ld, shb, clr, shp, ldp;
input [3:0] da, db;
output [7:0] p;

wire [3:0] gnd, a, qa, mux_out, add_out, qb;
wire cout;

assign gnd = 4'b0000; //connected to ground

dfffb u1(.clr(clr), .clk(clk), .ld(ld), .shb(shb), .db(db),.qb(qb));
dfffa u2(.clr(clr), .clk(clk), .ld(ld), .da(da), .qa(qa));
mux u3(.s(qb[0]), .a(gnd), .b(qa), .y(mux_out));
adder u4(.b(mux_out), .a(p[6:3]), .cout(cout), .sum(add_out));
preg u5(.cout(cout), .sum(add_out), .shp(shp), .ldp(ldp), .clr(clr), .p(p), .clk(clk));

endmodule

```

```

module top(da, db, p, clk, reset);
input [3:0] da, db;
input clk, reset;
output [7:0] p;

wire shb, ld, clr, ldp, shp;

mult u2(.da(da), .db(db), .p(p), .ld(ld), .shb(shb), .clr(clr), .clk(clk), .shp(shp), .ldp(ldp));
fsm u1(.reset(reset), .clk(clk), .shb(shb), .ld(ld),.clr(clr), .ldp(ldp), .shp(shp));

endmodule

```

```

module top_tb;
reg [3:0] da, db;
reg clk, reset;
wire [7:0] p;

top uut(.da(da), .db(db), .p(p), .clk(clk), .reset(reset));

initial clk = 0;
always
#10 clk = ~clk;

initial
begin
da = 4'b1011; db = 4'b1101; reset = 1;
#20
reset = 0;
#400 $stop;
end

endmodule

```



Pins Part 2.2 - Notepad


File Edit Format View Help

```
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz
```

```
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports { clk }];
```

```
set_property -dict { PACKAGE_PIN V10      IOSTANDARD LVCMOS33 } [get_ports { da[3] }]; |
set_property -dict { PACKAGE_PIN U11      IOSTANDARD LVCMOS33 } [get_ports { da[2] }]; |
set_property -dict { PACKAGE_PIN U12      IOSTANDARD LVCMOS33 } [get_ports { da[1] }]; |
set_property -dict { PACKAGE_PIN H6       IOSTANDARD LVCMOS33 } [get_ports { da[0] }]; |
set_property -dict { PACKAGE_PIN T13      IOSTANDARD LVCMOS33 } [get_ports { db[3] }]; |
set_property -dict { PACKAGE_PIN R16      IOSTANDARD LVCMOS33 } [get_ports { db[2] }]; |
set_property -dict { PACKAGE_PIN U8       IOSTANDARD LVCMOS33 } [get_ports { db[1] }]; |
set_property -dict { PACKAGE_PIN T8       IOSTANDARD LVCMOS33 } [get_ports { db[0] }]; |
set_property -dict { PACKAGE_PIN R13      IOSTANDARD LVCMOS33 } [get_ports { reset }];
```

```
set_property -dict { PACKAGE_PIN V16      IOSTANDARD LVCMOS33 } [get_ports { p[7] }]; |
set_property -dict { PACKAGE_PIN U16      IOSTANDARD LVCMOS33 } [get_ports { p[6] }]; |
set_property -dict { PACKAGE_PIN U17      IOSTANDARD LVCMOS33 } [get_ports { p[5] }]; |
set_property -dict { PACKAGE_PIN V17      IOSTANDARD LVCMOS33 } [get_ports { p[4] }]; |
set_property -dict { PACKAGE_PIN R18      IOSTANDARD LVCMOS33 } [get_ports { p[3] }]; |
set_property -dict { PACKAGE_PIN N14      IOSTANDARD LVCMOS33 } [get_ports { p[2] }]; |
set_property -dict { PACKAGE_PIN J13      IOSTANDARD LVCMOS33 } [get_ports { p[1] }]; |
set_property -dict { PACKAGE_PIN K15      IOSTANDARD LVCMOS33 } [get_ports { p[0] }];
```

 



### Result Discussion:

It took me a long time to get the 4 binary segmental multiplier multiplied values properly. I had issues mainly with mult and top. I also messed up the wiring a lot. The key findings of this part of the lab was how to put these components together and use sequential logic with the FSM to control all of these components. In this part of the lab, we figured out how to create shift registers and FSM and got complex circuits to work together. We had a multiplier on the FPGA that produces the correct values. The lab taught us a lot about how Verilog, Vivado and the NEXYS board works by setting pins and LEDs.

### Part 3: Character Display on 8-Digit Multiplexed Seven Segment Displays
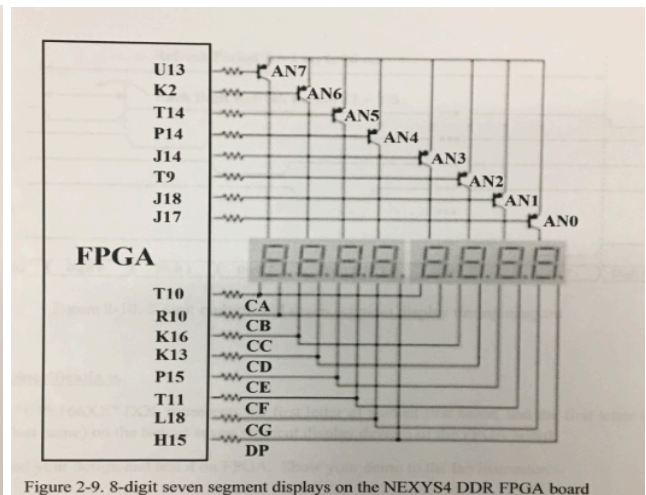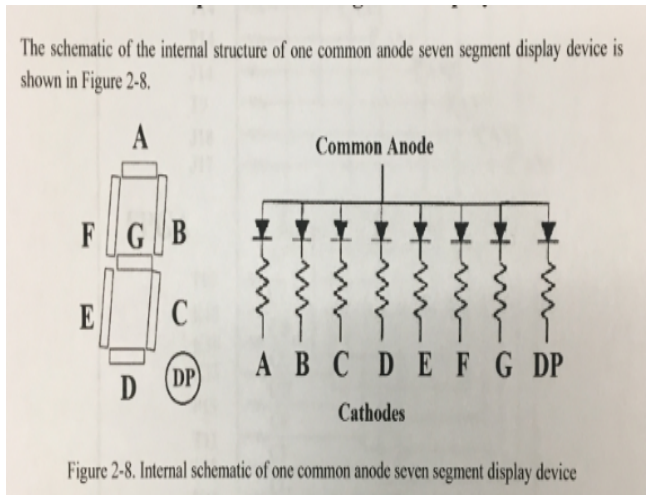
#### Part 3.1:

Here the anodes of the 7 segments are tied together as AN7, AN6, AN5, AN4, AN3, AN2, AN1, and AN0. For the cathodes they remain separated as CA, CB, CC, CD, CE, CF, CG, and DP. The FPGA drives the anode signals and corresponding cathode patterns of each digit in continuous fast-paced signals.



## Part 3.2:

### Source Code:

```

module fpga(clk, seg, dig);
input clk;
output [7:0] seg;
output [7:0] dig;

parameter N = 18;

reg [ N-1: 0] count;
reg [3:0] dd;
reg [7:0] seg;
reg [7:0] an;

always @(posedge clk)
begin
    count <= count + 1;

    case(count[N-1:N+3])
        3'b000:
            begin
                dd = 4'd7;
                an = 8'b11111110;

            end
        3'b001:
            begin
                dd = 4'd6;
                an = 8'b11111101;

            end
        3'b010:
            begin
                dd = 4'd5;
                an = 8'b111111011;

            end
        3'b011:
            begin
                dd = 4'd4;
                an = 8'b11110111;

            end
        3'b100:
            begin
                dd = 4'd3;
                an = 8'b11101111;

            end
        3'b101:
            begin
                dd = 4'd2;
                an = 8'b11011111;

            end
        3'b110:
            begin
                dd = 4'd1;
                an = 8'b10111111;

            end
        3'b111:
            begin
                dd = 4'd0;
                an = 8'b01111111;

            end
    endcase
    assign dig = an;

    always @ (dd)
    begin
        seg[7] = 1'b1;
        case(dd)
            4'd0: seg[6:0] = 7'b1000110 //display C
            4'd1: seg[6:0] = 7'b0001100 //display P
            4'd2: seg[6:0] = 7'b0000110 //display E
            4'd3: seg[6:0] = 7'b1111001 //display 1
            4'd4: seg[6:0] = 7'b0000010 //display 6
            4'd5: seg[6:0] = 7'b0000010 //display 6
            4'd6: seg[6:0] = 7'b0001000 //display A
            4'd7: seg[6:0] = 7'b1000110 //display C

            default: seg[6:0] = 7'b1111111; //blank
        endcase
    end
endmodule

```

```

set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz

create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports { clk }];

set_property -dict { PACKAGE_PIN T10     IOSTANDARD LVCMOS33 } [get_ports { seg[0] }]; #IO_L24N_T3_A00_D16_14 Sch=ca
set_property -dict { PACKAGE_PIN R10     IOSTANDARD LVCMOS33 } [get_ports { seg[1] }]; #IO_25_14 Sch=cb
set_property -dict { PACKAGE_PIN K16     IOSTANDARD LVCMOS33 } [get_ports { seg[2] }]; #IO_25_15 Sch=cc
set_property -dict { PACKAGE_PIN K13     IOSTANDARD LVCMOS33 } [get_ports { seg[3] }]; #IO_L17P_T2_A26_15 Sch=cd
set_property -dict { PACKAGE_PIN P15     IOSTANDARD LVCMOS33 } [get_ports { seg[4] }]; #IO_L13P_T2_MRCC_14 Sch=ce
set_property -dict { PACKAGE_PIN T11     IOSTANDARD LVCMOS33 } [get_ports { seg[5] }]; #IO_L19P_T3_A10_D26_14 Sch=cf
set_property -dict { PACKAGE_PIN L18     IOSTANDARD LVCMOS33 } [get_ports { seg[6] }]; #IO_L4P_T0_D04_14 Sch=cg
set_property -dict { PACKAGE_PIN H15     IOSTANDARD LVCMOS33 } [get_ports { seg[7] }]; #IO_L19N_T3_A21_VREF_15 Sch=dp

set_property -dict { PACKAGE_PIN J17     IOSTANDARD LVCMOS33 } [get_ports { dig[0] }]; #IO_L23P_T3_F0E_B_15 Sch=an[0]
set_property -dict { PACKAGE_PIN J18     IOSTANDARD LVCMOS33 } [get_ports { dig[1] }]; #IO_L23N_T3_FWE_B_15 Sch=an[1]
set_property -dict { PACKAGE_PIN T9      IOSTANDARD LVCMOS33 } [get_ports { dig[2] }]; #IO_L24P_T3_A01_D17_14 Sch=an[2]
set_property -dict { PACKAGE_PIN J14     IOSTANDARD LVCMOS33 } [get_ports { dig[3] }]; #IO_L19P_T3_A22_15 Sch=an[3]
set_property -dict { PACKAGE_PIN P14     IOSTANDARD LVCMOS33 } [get_ports { dig[4] }]; #IO_L8N_T1_D12_14 Sch=an[4]
set_property -dict { PACKAGE_PIN T14     IOSTANDARD LVCMOS33 } [get_ports { dig[5] }]; #IO_L14P_T2_SRCC_14 Sch=an[5]
set_property -dict { PACKAGE_PIN K2      IOSTANDARD LVCMOS33 } [get_ports { dig[6] }]; #IO_L23P_T3_35 Sch=an[6]
set_property -dict { PACKAGE_PIN U13     IOSTANDARD LVCMOS33 } [get_ports { dig[7] }]; #IO_L23N_T3_A02_D18_14 Sch=an[7]

```

### Result Discussion:

I managed to manipulate the 7-segment display. This lab was pretty easy with no issues. The code was already given to us online. I just had to understand how to configure the pins and manipulate the bytes so that the LED can light my initials. The goal of this part was how to write constraint files as well as how the anodes and diodes work with the seven-segment display to show values. It also helped us get familiar with the Vivado program and FPGA.

## **Conclusion**

In conclusion, this lab helped me learn more about Verilog. It taught me how to code with hierarchy design and writing testbenches. I also got a better understanding of how waveforms are read and how to use it to check if our code was correct. The first part was simple. Create each circuit design and connect them at the end. Part 2 then introduced us to sequential design with the FSM. This part was the hardest for me. I struggled getting the right output. Part 3 taught us how to use a multiplexed seven segment display. Overall, This lab really gave me a better understanding of how coding in Verilog works and the steps to creating a circuit. It also helped to use the FPGA and seven segment display to see how the software and hardware interact with each other.